

Solution

College of Technological Studies, Electronics Department
Electrical Circuits (ENT#140)

Final Exam


Name: _____

Date: _____

Problem-1:

For the circuit shown below, to calculate the following:

1. V_1 .
2. V_3 .
3. V_{ab} .
4. I_s .

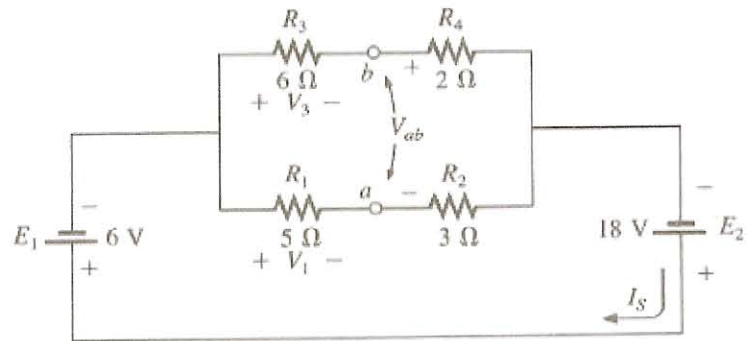

Solution-1:

$$1) V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(5\Omega) \times (12V)}{(5\Omega) + (3\Omega)} = \frac{60V}{8\Omega} = 7.5V \Rightarrow \boxed{V_1 = 7.5V}$$

$$2) V_3 = \frac{R_3 E}{R_3 + R_4} = \frac{(6\Omega) \times (12V)}{(6\Omega) + (2\Omega)} = \frac{72V}{8\Omega} = 9V \Rightarrow \boxed{V_3 = 9V}$$

From the simple figure, with clockwise direction starting at terminal a

$$\therefore +V_1 - V_3 + V_{ab} = 0 \leftarrow (\text{KVL})$$

$$V_{ab} = V_3 - V_1 \Rightarrow V_{ab} = 9V - 7.5V = 1.5V \Rightarrow \boxed{V_{ab} = 1.5V}$$

By Ohm's Law

$$I_1 = \frac{V_1}{R_1} = \frac{7.5V}{5\Omega} = 1.5A \Rightarrow \boxed{I_1 = 1.5A}$$

$$I_3 = \frac{V_3}{R_3} = \frac{9V}{6\Omega} = 1.5A \Rightarrow \boxed{I_3 = 1.5A}$$

$$\text{By (KCL)} \quad I_s = I_1 + I_3 \Rightarrow I_s = (1.5A) + (1.5A) = 3A$$

$$\boxed{I_s = 3A}$$

Solution

College of Technological Studies, Electronics Department
Electrical Circuits (ENT#140)

Final Exam


Name: _____

Date: _____

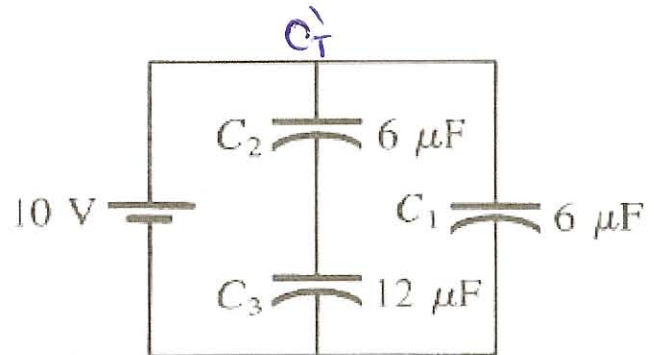Problem-2:

Find the voltage across and charge on each capacitor for the circuit shown below.

This is mean to calculate the following: V and Q on the C_1 , C_2 and C_3 .



Solution-2:

$$C = \frac{Q}{V} \Rightarrow C_T' = \frac{C_2 \times C_3}{C_2 + C_3} = \frac{6 \times 12}{6 + 12} = 4 \mu F \Rightarrow \boxed{C_T' = 4 \mu F}^*$$

$$\Rightarrow Q_T' = Q_2 = Q_3 \Rightarrow Q_T' = C_T' \cdot V = (4 \mu F) \times (10V) = 40 \mu C$$

$$\boxed{Q_T' = 40 \mu C}^*$$

$$\Rightarrow V_2 = \frac{Q_T'}{C_2} = \frac{40 \mu C}{6 \mu F} = 6.67 V \Rightarrow \boxed{V_2 = 6.67 V}^*$$

$$V_3 = \frac{Q_T'}{C_3} = \frac{40 \mu C}{12 \mu F} = 3.33 V \Rightarrow \boxed{V_3 = 3.33 V}^*$$

$$Q_1 = C_1 V_1 = (6 \mu F) \times (10V) = 60 \mu C$$

$$\boxed{Q_1 = 60 \mu C}^*$$

Solution

Final Exam


Name: _____

Date: _____

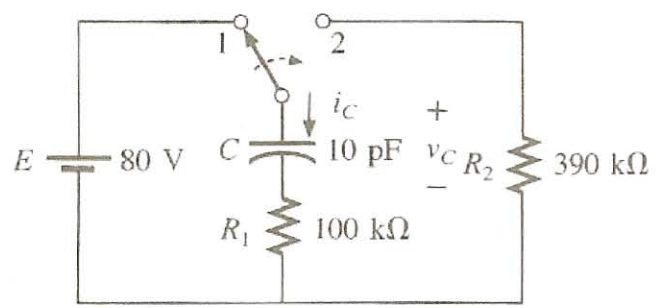Problem-3:

For the network shown below:

- Find the mathematical expression for the voltage across the capacitor after the switch is thrown into position 1.
- Repeat part (a) for the current i_C .
- Find the mathematical expressions for the voltage v_C and current i_C if the switch is thrown into position 2 at a time equal to five time constants of the charging circuit.
- Plot the waveforms of v_C and i_C for period of time extending from $t=0$ to $t=30\mu s$.



$$\tau = R \cdot C \Rightarrow \tau = (100 \times 10^3) \times (10 \times 10^{-12})$$

$$\tau = 1 \mu s$$

Position 1 Solution-3:

$$V_C = E (1 - e^{-t/\tau})$$

$$V_C = 80 (1 - e^{-t/1\mu s})$$


$$V_C = 80 (1 - e^{-t/1 \times 10^{-6} s})$$

$$i_C = \frac{E}{R} e^{-t/\tau}$$

$$i_C = \frac{80V}{100 \times 10^3 \Omega} e^{-t/1 \times 10^{-6} s}$$

$$i_C = 8 \times 10^{-4} e^{-t/1 \times 10^{-6} s}$$

Draw just approximately +

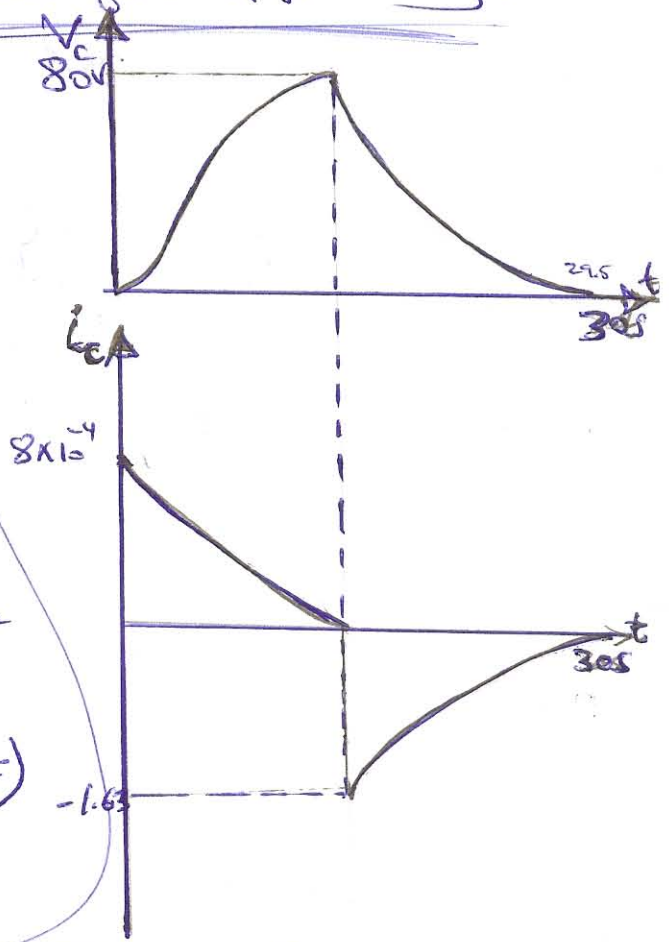

Position 2:

$$R_T = R_1 + R_2 \Rightarrow R_T = 100k\Omega + 390k\Omega$$

$$R_T = 490k\Omega$$

$$\tau' = R_T \cdot C \Rightarrow \tau' = (490k\Omega) \times (10 \times 10^{-12} F)$$

$$\tau' = 4.9 \times 10^{-6} s$$

Discharge phase

$$V_C = E e^{-t/\tau'}$$

$$V_C = 80V e^{-t/4.9 \times 10^{-6} s}$$

$$i_C = -I_C e^{-t/\tau'} \Rightarrow i_C = \frac{-80}{490k\Omega} e^{-t/4.9 \times 10^{-6} s}$$

$$i_C = -1.63 \times 10^{-4} e^{-t/4.9 \times 10^{-6} s}$$

Solution

College of Technological Studies, Electronics Department
Electrical Circuits (ENT#140)

Final Exam

Name: _____

Date: _____

Problem-4:


For the network shown below:

- Determine the mathematical expression for the current i_L and voltage v_L after the switch is closed.
- Repeat part (a) if the switch is opened after a period of five time constants has passed.

$$\textcircled{a} I_m = \frac{20}{10k} = 2 \text{ mA}$$

$$\therefore i_L = 2 \text{ m} (1 - e^{-t/\tau})$$
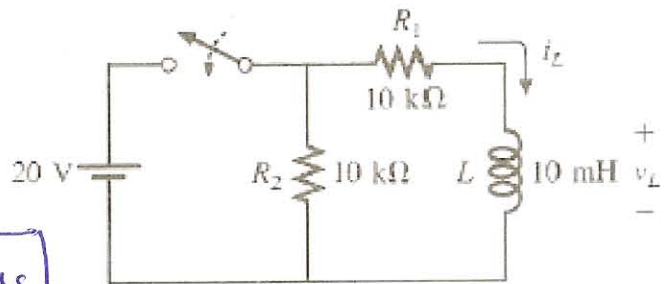
$$\tau = \frac{L}{R} = \frac{10 \text{ m}}{10k} = 1 \mu\text{s} \rightarrow \boxed{\tau = 1 \mu\text{s}}$$





Solution-4:

⑥ Switch is opened after $t = 5\tau$

$$\tau = \frac{L}{R_1 + R_2} = \frac{10 \text{ m}}{20k} = 0.5 \mu\text{s}$$

$$i_L = 2 \text{ m} e^{-t/0.5 \mu\text{s}}$$
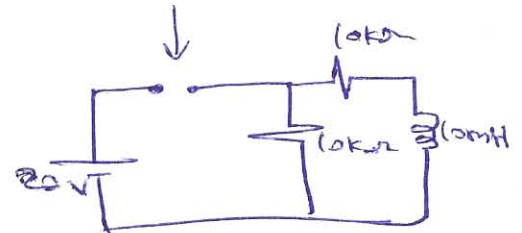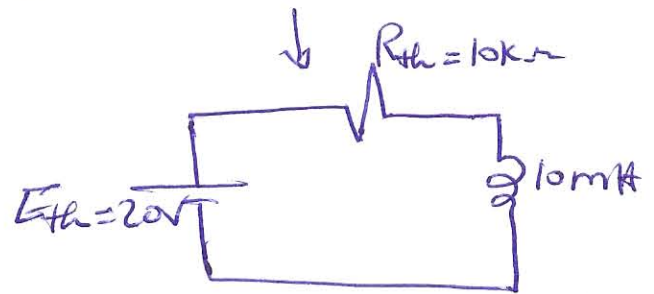
$$v_L = E \left(1 + \frac{R_2}{R_1} \right) \cdot (1 - e^{-t/\tau})$$



$$v_L = 20(1 + 1) \cdot (1 - e^{-t/\tau}) = 40(1 - e^{-t/\tau})$$

$$\boxed{v_L = 40(1 - e^{-t/\tau})}$$

Solution

College of Technological Studies, Electronics Department
Electrical Circuits (ENT#140)

Final Exam

Name: _____

Date: _____

Problem-5 [Additional Point]:


For the network shown below:

- Find the mathematical expression for the current i_L and voltage v_L after the switch is closed.
- Find the mathematical expressions for the voltage v_L and current i_L if the switch is opened after a period of five time constants has passed.
- Plot the waveforms of v_L and i_L for the time period defined by parts (a) and (b).
- Sketch the waveform for the defined polarities and directions.
- Find the current through the inductor after it is reached its final value.

$$\tau = \frac{L}{R_1} = \frac{5 \times 10^{-3}}{6.8 \times 10^3} = 0.73 \mu s$$


Solution-5:

a) i_L, v_L when S is closed \rightarrow

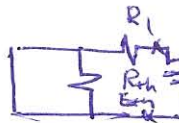

$$R_{th} = R_1 = 6.8 k\Omega$$

$$E_{th} = 6V$$

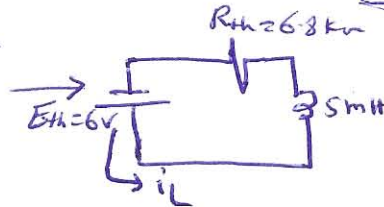




$$i_L = \frac{E_{th}}{R_{th}} (1 - e^{-t/\tau})$$

$$I_m = \frac{E_{th}}{R_{th}} = \frac{6V}{6.8k\Omega} = 0.88 mA$$

$$\tau = \frac{L}{R_{th}} = \frac{5m}{6.8k} = 0.735 \mu s$$

$$i_L = 0.88 (1 - e^{-t/0.735 \mu s})$$

$$v_L = 6e^{-t/0.735 \mu s}$$

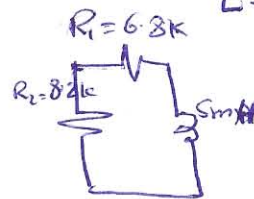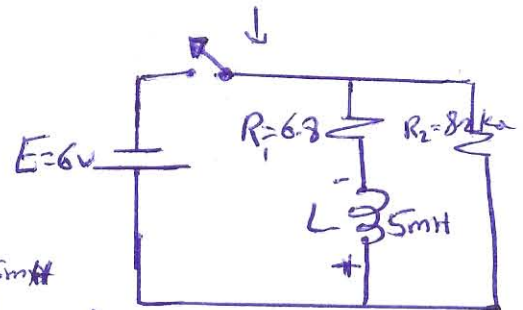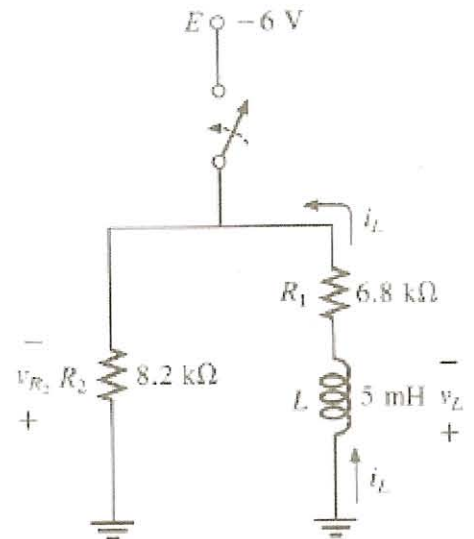

b) If S is opened after 5 τ

$$\tau_2 = \frac{L}{(R_1 + R_2)} = \frac{5m}{(6.8k + 8.2k)} = \frac{5m}{15k}$$

$$\tau_2 = \frac{5m}{15k} \Rightarrow \tau_2 = 0.333 \mu s$$

$$v_L = V_i (1 - e^{-t/\tau_2}) \Rightarrow v_L = E (1 + \frac{R_1}{R_2})$$

$$v_L = 6 (1 + \frac{8.2}{6.8}) = 13.23 V$$

$$v_L = 13.23 (1 - e^{-t/0.333 \mu s})$$

$$i_L = I_m e^{-t/\tau_2} \Rightarrow i_L = 0.88 mA e^{-t/0.333 \mu s}$$

